

## > Basic gates

### 1) AND gate

o/p is high only if all inputs are high




Boolean eq<sup>n</sup>:  $A \cdot B$

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1
 
### 2) OR gate

o/p is high ~~or~~ if atleast one i/p is high



Boolean eq<sup>n</sup>:  $A + B$

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

### 3) NOT gate

it inverts the binary i/p  
i.e o/p is the opposite of the i/p.




Boolean eq<sup>n</sup> :  $\bar{A}$

A	$\bar{A}$
0	1
1	0

### > Universal gates

#### 1) NAND gate

o/p is low only when all inputs are high

 

Boolean eq<sup>n</sup> :  $\bar{A} \cdot \bar{B}$

A	B	$\bar{A} \cdot \bar{B}$
0	0	1
0	1	1
1	0	1
1	1	0

2) NOR gate

o/p is high only when all inputs are low



Boolean eq<sup>n</sup> :  $\overline{A+B}$

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

> EX-OR gate (Exclusive OR) / XOR  
o/p is high only when inputs are different.




Boolean eq<sup>n</sup> :  $A \oplus B = A\bar{B} + \bar{A}B$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


if  $A = B \Rightarrow$  o/p is low

if  $A \neq B \Rightarrow$  o/p is high

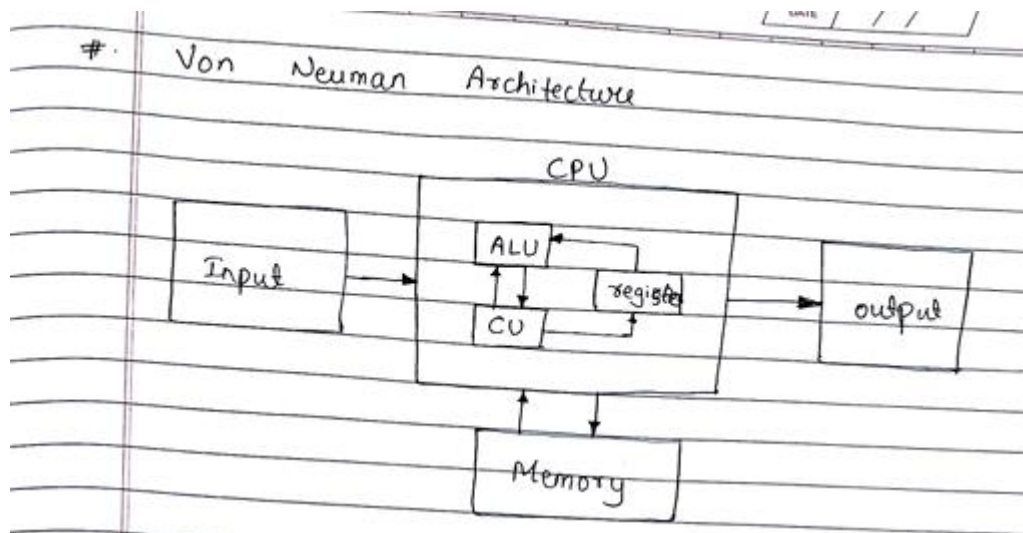

## Difference between Restoring and Non-Restoring Division Algorithms

Point	Restoring Division	Non-Restoring Division
1. Procedure	If subtraction gives a negative result, the divisor is <b>restored</b> (added back) in the next step.	If subtraction gives a negative result, no restoring is done — instead, correction happens in the next cycle.
2. Complexity	Needs <b>extra step</b> for restoring the remainder, so more operations.	Faster since it avoids restoring steps.
3. Hardware	Simpler control logic but requires <b>more steps</b> .	Slightly more complex control logic but <b>fewer steps overall</b> .
4. Speed	<b>Slower</b> due to restoring after negative remainders.	<b>Faster</b> as it directly adjusts in the next iteration.
5. Usage	Easier to understand and implement, mostly used for teaching and simple hardware.	Preferred in modern processors due to efficiency.

 

It is a computer architecture where **program instructions and data are stored in the same memory** and accessed through a single bus.

◆ Key points:

- Uses **stored-program concept**.
- Single memory for **data + instructions**.
- Consists of **CPU (ALU + Control Unit), Memory, and I/O**.
- Executes instructions **sequentially (fetch → decode → execute)**.